

## Ch. 14 - Making and Using Electricity

### L. 1 - What is electricity? - page 474

#### 1. static electricity

- an electrical charge that builds up on an object

#### 2. current electricity


- a steady stream of charges (electrons)
- an electric current moves through a material such as a copper wire

#### 3. circuit


- the close path that an electric current follows
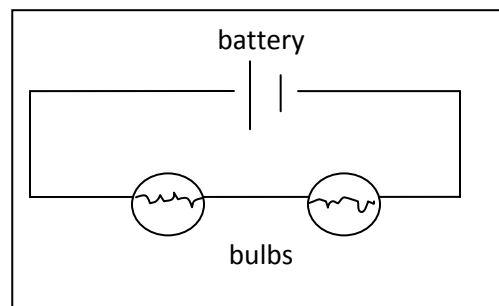
#### 4. series circuit

- only one path for current to follow
- if one part fails (breaks) it opens the circle and it doesn't work
- working series circuit



- open series circuit

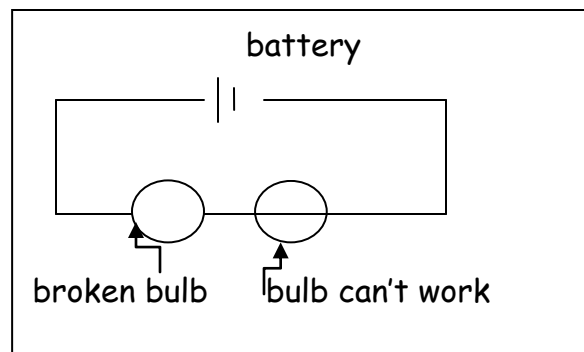


## Ch. 14 - Making and Using Electricity

### L. 1 - What is electricity? - page 474
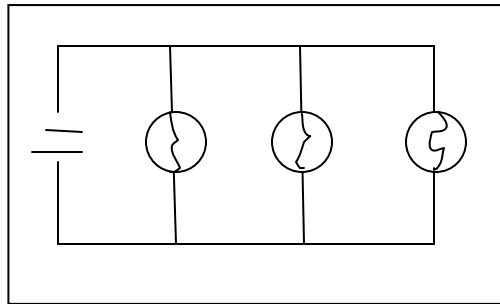
#### 5. parallel circuit

- more than one path for the electric current to follow
- if one path fails (breaks) the current can travel along another path and keep working



#### 6. conductors

- materials that let electric charges move through them easily
- close circuits
- examples:
  - \*most metals
  - \*copper
  - \*salt water

#### 7. insulators

- materials that do NOT let electric charges move easily through them
- opens circuits
- examples:
  - \*plastic
  - \*rubber
  - \*glass
  - \*wood


#### 8. switch

- a device that opens or closes a current

## Ch. 14 - Making and Using Electricity
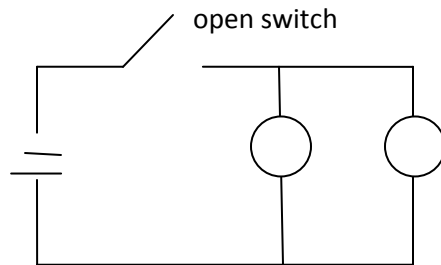
### L. 1 - What is electricity? - page 474

- an open switch can open even a parallel series - because it leaves no closed path



- this open switch still leaves one path that will carry the electrons

