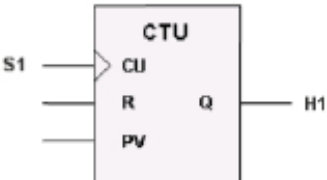
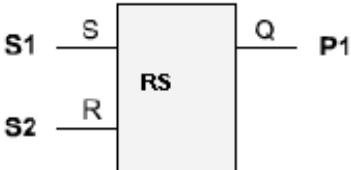
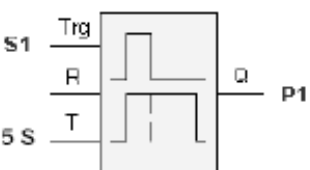
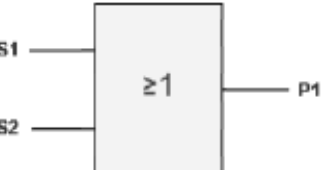
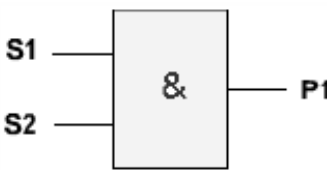


Q1: Match the following tasks with the proper function blocks:


	Task		Function Blocks
1	Turn ON a machine when the PB is pressed and the machine door is closed	2	
2	Count the number of produced Cola cans	4	
3	Switch OFF a machine after a certain time	3	
4	Turn ON and Turn OFF a motor using the same function block	5	
5	Turn ON a lamp using either PB1 or PB2 or both	1	

Q2: For the following tasks write the correct expressions and draw the Function Block Diagrams:

a) A pump (P) turns ON when (PB1) is pressed and it turns OFF When (PB2) is pressed


$$P = PB1$$

$$\overline{P} = PB2$$

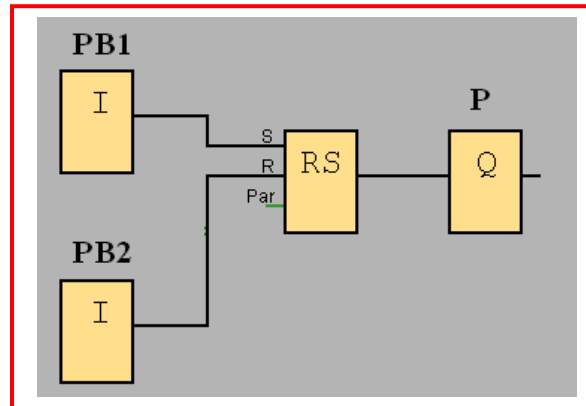


b) A light (L1) turns ON when (S1) is switched ON and (S2) is switched OFF.

$$L = S1 \cdot \overline{S2}$$

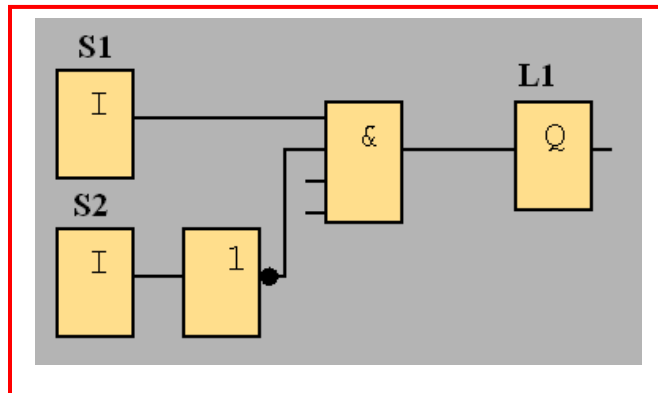


c) A green light (Q1) turns on when both (S1) and (S2) are switched ON or (S3) is switched ON

$$Q1 = S1 \cdot S2 + S3$$

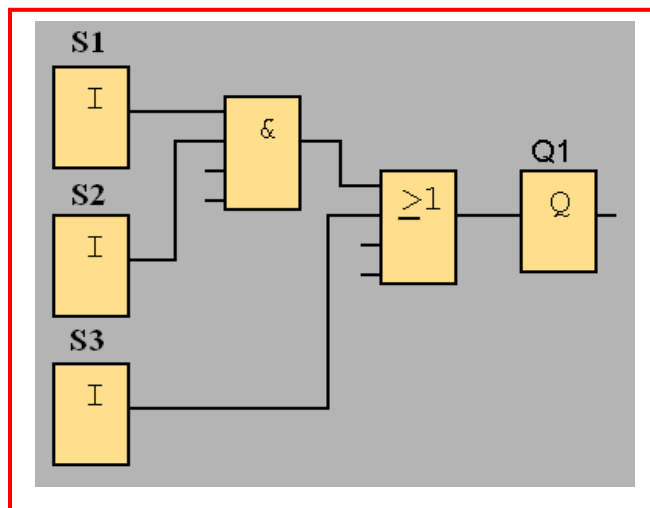


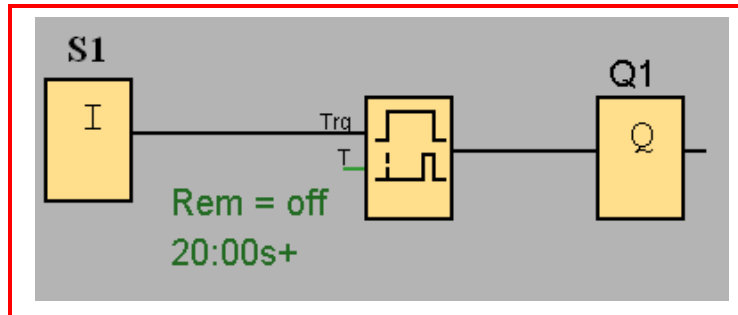d) A machine (Q1) starts 20 seconds after switching ON (S1), it keeps running until (S1) is switch OFF.




Q3: For the following FBDs write the correct expression:

a)

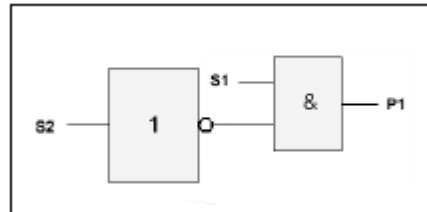


$$P1 = S1 \cdot \overline{S2}$$

b)

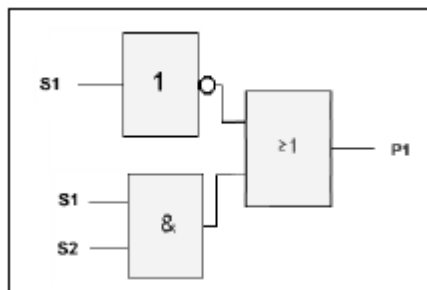

$$P1 = \overline{S1} + (S1 \cdot S2)$$

c)

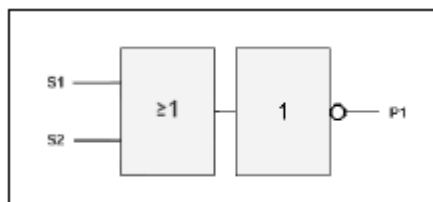

$$P1 = \overline{S1 + S2}$$