

Complete the wiring for a LOGO! PLC application in which lamp L1 must be ON if switch S1 or switch S2 is pressed, and lamp L2 must be OFF if switch S2 is pressed. Also draw the function Block Diagram.

S1 : I1

L1 : Q1

S2 : I2

L2: Q2

