

Ladder Diagrams

Ladder Diagrams


Logic gates

Truth tables

1. Output bit 0 in IO Simulator matches Q5 in PLC. (1 point)

- ☐ True
- ☐ False

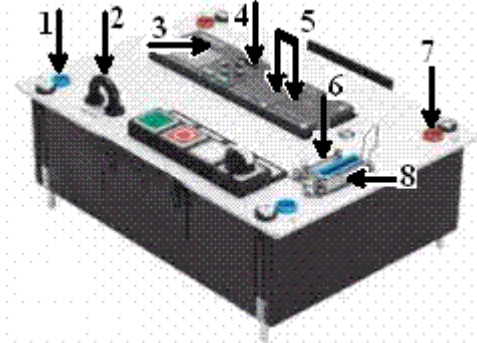2. Match The LOGO! EduTrainer components and names: (16 points)



- a. 24 VDC socket
- b. Two expansion modules
- c. EMERGENCY-STOP bridge
- d. 0 VDC socket
- e. Submini-D socket
- f. SysLink interface
- g. LOGO! Basic
- h. Interface unit


3. For OFF Delay timer the output isuntil a defined time has expired. (1 point)
- _____

4. For LOGO PLC one of the following sockets is used for analogue signal: (2 points)

- ☐ Interface socket
- ☐ Submini-D socket
- ☐ SysLink socket
- ☐ 24 VDC socket

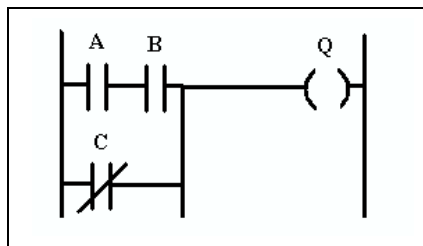5. The following diagram is called: (2 points)

- ☐ Circuit diagram
- ☐ Logic gates diagram
- ☐ Ladder diagram
- ☐ Function Block Diagram



6. InAn input pulse increments or decrements an internal value, depending on the parameter setting (1 point)

7. Which one of the following is NOT contact (Break Contact): (2 points)

☐ --| |--

☐ --(\)--

☐ --|\--

☐ --()--


8. To insert a time delay relay SF must be selected. (1 point)

☐ True

☐ False

9. For ON dealy timer The output is until a configured delay time has expired. (1 point)

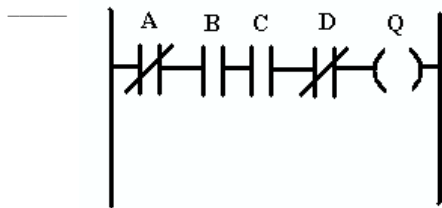10. Match each of the following Ladder Diagrams with the correct logical expression: (20 points)



a. $(\bar{A}.B)+(C+D)$

b. $(\bar{A}.B).(C.\bar{D})$

c. $(\bar{A}.B)+\bar{C}$

d. $(\bar{A}.B)+(C.\bar{D})$

e. $(A.B)+(C.D)$





f. $(A.B).(C+D)$






g. $(\bar{A}.B).(C+\bar{D})$

h. $(A+B).\bar{C}$

i. $(A.B)+\bar{C}$

j. $A.B.\bar{C}$

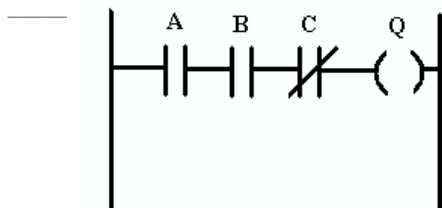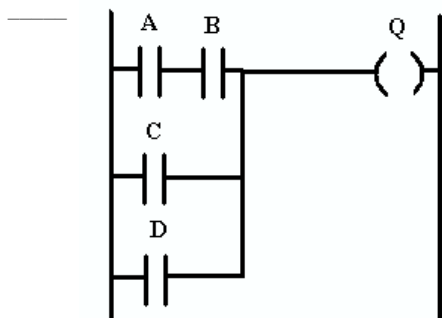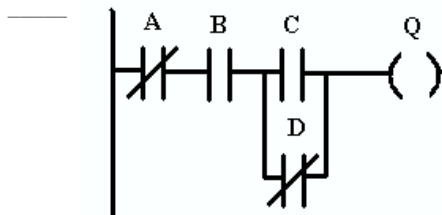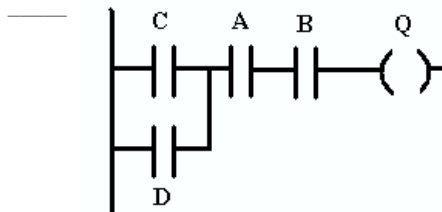

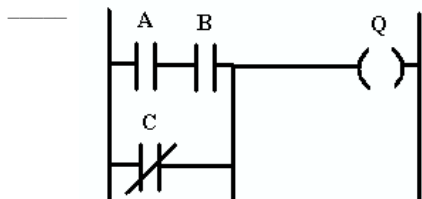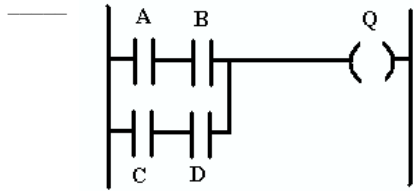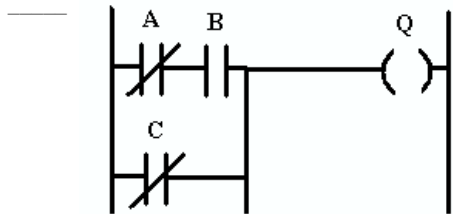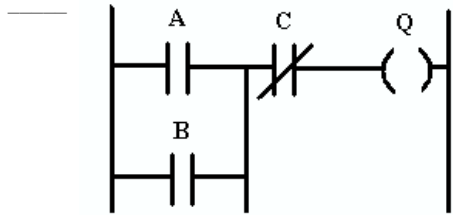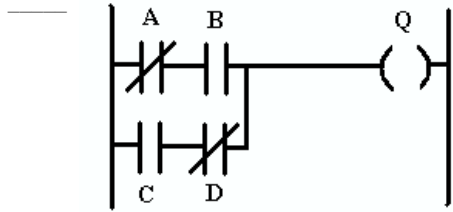

11. The given truth table represents : (2 points)

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

- ☐ AND gate
- ☐ OR gate
- ☐ NAND gate
- ☐ NOT gate
12. Hours Counter may widely be used for scheduling
(1 point)
-
13. The controller which is able to work in sever conditions is: (2 points)
- ☐ Computer
- ☐ PLC
- ☐ Microcontroller
- ☐ Microprocessor
14. The reason(s) why we need Hardware Controller is (are): (2 points)
- ☐ To reduce time
- ☐ To increase the quality
- ☐ To allow for change
- ☐ All answers are correct

Ladder Diagrams

Ladder Diagrams

Logic gates

Truth tables

1. True
2. d, c, g, h, b, e, f, a
3. not reset, ON
4. Submin-D socket
5. Ladder diagram
6. Up/Down Counter, up down counter, counter
7. --|\|--
8. True
9. not switched on, off
10. b, f, g, a, j, d, h, c, e, i
11. AND gate
12. maintenance
13. PLC
14. All answers are correct